

## Chapter 1

# Electricity Worksheet

You have a Battery, two pieces of wire, and a light bulb. Make the bulb turn on.